
Inside view of torch

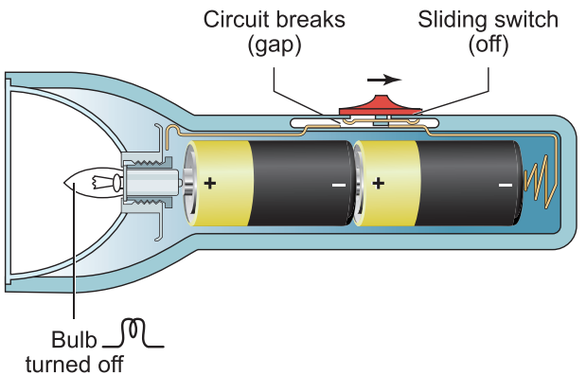

An **electric circuit** is the continuous or unbroken closed path along which electric current flows from the positive terminal to the negative terminal of the battery. A circuit generally has:

a) **A cell are battery**- a source of electric current


b) **Connecting wires**- for carrying current

c) **A bulb**- a device that consumes the electricity


d) **A key or a switch**- this may be connected anywhere along the circuit to stop or allow the flow of current.

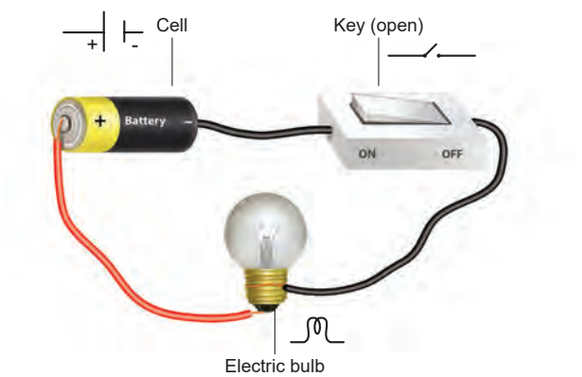a. Open Circuit

In a circuit if the key is in open (off) condition, then electricity will not flow and the circuit is called an open circuit. The bulb will not glow in this circuit.



b. Closed Circuit

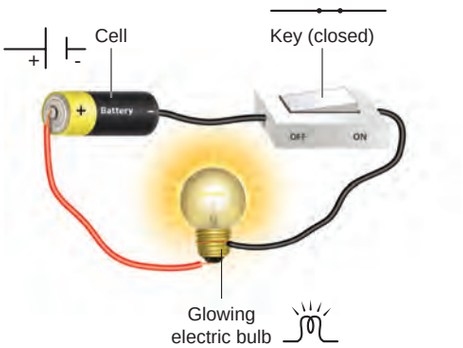

In a circuit if the key is in closed (on) condition, then electricity will flow and the circuit is called a closed circuit. The bulb will glow in this circuit.

Can you make a simple switch own by simple things available to you?


Types of Circuits

1. **Simple Circuit**
2. **Series Circuit**
3. **Parallel Circuits**

A1VYPV

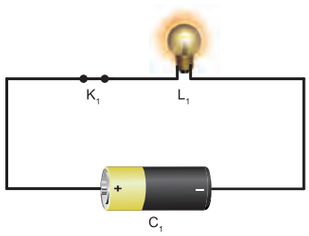1. Simple Circuit

A circuit consisting of a cell, key, bulb and connecting wires is called a simple circuit.



2. Series Circuit

If two or more bulbs are connected in series in a circuit, then that type of circuit is called series circuit. If any one of the bulbs