
Arrange copper and zinc plates in series as shown in the figure. Half fill two beakers with porridge. Connect the copper plate with the positive of and LED bulb and zinc to the negative. Observe what happens.

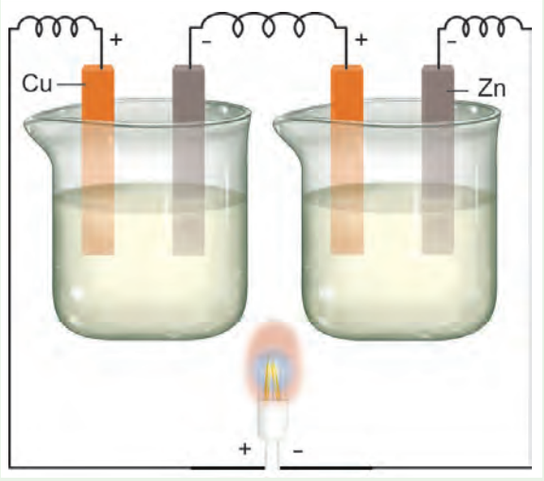Now you can replace porridge with curd, potato, lemon etc.



A1ZLDS

Points to remember

- Any device from which electricity is produced, is called the source of electricity.
- There are many sources of electricity such as thermal power stations, hydel electric power stations, wind mills, atomic power station etc.
- Device that converts chemical energy into electrical energy is called a cell.
- Electric cells are of two types depending on the continuity of flow of electric current.
- Primary cell is a cell that is designed to be used once and discarded.
- A cell that can be recharged many times is called secondary cell.
- Two or more cells combined together to make a battery.
- An electric circuit is the continuous or unbroken closed path along with electric current flows from the positive terminal to the negative terminal of the battery.
- A circuit consisting of a cell, key, bulb and connecting wires is called a simple circuit
- If two or more bulbs are connected in series in a circuit, then that type of circuit is called series circuit.
- If two or more bulbs are connected in parallel in a circuit, then that type of circuit is called parallel circuit.
- Symbols of electrical components are used to represent complicated circuits in simple way.
- The materials which allow electric charges to pass through them are called conductors.
- The materials which do not allow electric charges to pass through them are called insulators or non-conductors.

6th Science_IInd Term English Book_Unit_2.indd 26 25-03-2019 12.12.44 PM