Evaluation

A25URI

I. Choose the appropriate answer

1. The device which converts chemical energy into electrical energy is

   a. fan b. solar cell

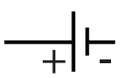
   c. cell d. television

2. Electricity is produced in

   a. transformer b. power station

   c. electric wire d. television

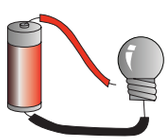
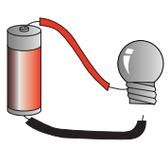
3. Choose the symbol for battery

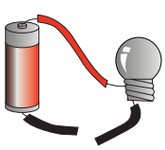
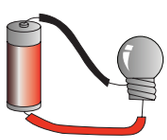
a.  b. 

c. 

d.

4. In which among the following circuits does the bulb glow?

a.  b. 

c.  d. 

5. _____ is a good conductor

   a. silver b. wood

   c. rubber d. plastic

II. Fill in the blanks

1. _____ are the materials which allow electric current to pass through them.
2. Flow of electricity through a closed circuit is _____.
3. _____ is the device used to close or open an electric circuit.
4. The long perpendicular line in the electrical symbol represents its _____ terminal.
5. The combination of two or more cells is called a _____.

III. True or False. If False, give the correct statement

1. In a parallel circuit, the electricity has more than one path.
2. To make a battery of two cells, the negative terminal of one cell is connected to the negative terminal of the other cell.
3. The switch is used to close or open an electric circuit.
4. Pure water is a good conductor of electricity.
5. Secondary cell can be used only once.

IV . Match the following

sl.no.	Symbol	Description
1		open key
2		cell
3		bulb glows
4		battery
5		bulb does not glow

6th Science_IInd Term English Book_Unit_2.indd 29 25-03-2019 12.12.46 PM